

EE518 Analog IC-DESIGN LAB
Experiment 3

**Design and analysis of various current mirror
circuits.**



Submitted by,
KOTAPATI VAMSHI KRISHNA
ROLL No-234102412
MTECH IN VLSI AND NANOELECTRONICS
September 2, 2024

Contents

1	EXPERIMENTS	2
2	OBJECTIVE	2
3	Theory	2
3.1	Theory for current mirror circuits	2
3.2	Cascoded mirror circuit	3
3.3	High voltage swing current mirror circuit	4
4	Schematic and graphs	5
4.1	Basic current mirror circuit	5
5	Basic current mirror circuit with $3I_{ref}$	7
6	Basic current mirror circuit with $1/3 I_{ref}$	9
7	Multiple finger based current mirror circuits	11
8	Cascoded current mirror circuit	15
9	High swing cascoded current mirror circuit	17
10	Comparison table	19
11	Conclusions:-	19

1 EXPERIMENTS

Design and analysis of various current mirror circuits.

2 OBJECTIVE

- Basic current mirror circuit with $(W/L) = (0.36/0.18)$ to generate $(3I_{ref})$ and one third of the reference current $(1/3 I_{ref})$.
- Multiple finger based current mirror circuit.
- Normal cascode current mirror circuit.
- High swing cascode current mirror circuit.

3 Theory

3.1 Theory for current mirror circuits

A current mirror circuit is used to copy one active device's input current to the output of other active devices. Here, the flow of current can be copied in the form of inverting from device to device. Once the flow of current within the first active device is altered then the reflected output current from the other active device will also be changed. the designing of current mirror circuits can be done with two main transistors. it copies the flow of current in one active device whereas, in another active device, it maintains the output current stable instead of loading. The copied current is a constant current.


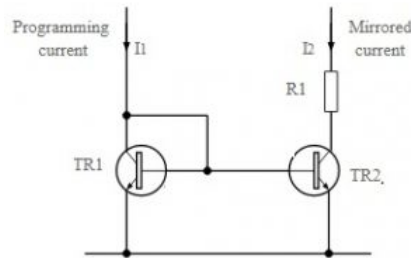


Figure 1: Basic current mirror circuit

the current flowing through the MOSFETs must be equal if the width and length are equal, assumes negligible channel length modulation. However, this is not always the case in applications. Current mismatch can be caused by some faults such as process change, VDS difference and VTH mismatch.

In basic current mirror circuit we make both gate to source voltages are same, but we didn't know both drain to source voltage are same. so we are going to build a cascode structure on top of the copy mosfet. so we know that cascode circuit is make drain voltage not vary from the changes from load. also we need to make sure cascode circuit also in saturation. Therefore, we create the same cascode circuit on top of the reference MOSFET as well, connecting it as a diode and connecting the gate source voltage to the copy circuit's cascode.

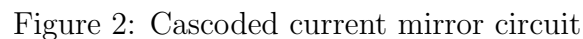

3.3 High voltage swing current mirror circuit

A current mirror may also be characterized as having an output voltage swing. High voltage swing in current mirrors is desired for accurate operation with low power supply voltages and for increased voltage signal amplitudes which improve the accuracy of analog circuitry utilizing the current mirrors. We received the VDS effect, not the current copy. However, it reduces the drain to source voltage swing, which is the lowest value, and $2V_{DSAT} - V_{th}$. We are therefore going to set the reference cascode gate to source voltage equal to $2V_{DSAT} + V_{th}$ in order to maximize the swing, and we will copy the cascode mosfet with a minimum drain to source voltage of $2V_{DSAT}$.

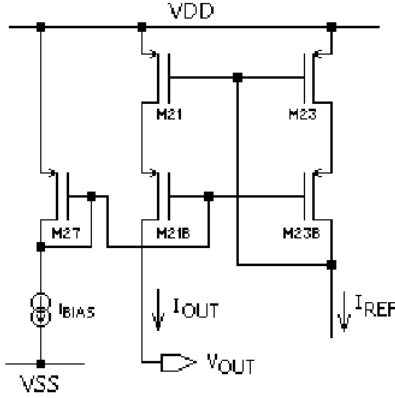


Figure 3: High voltage swing Cascoded current mirror circuit

4 Schematic and graphs

4.1 Basic current mirror circuit

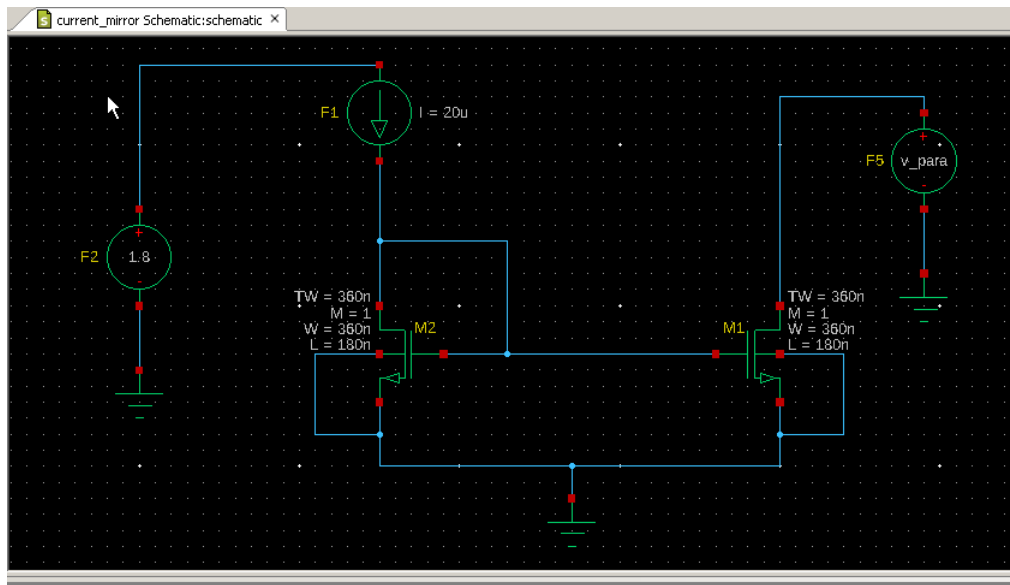


Figure 4: circuit diagram for Basic current mirror circuit

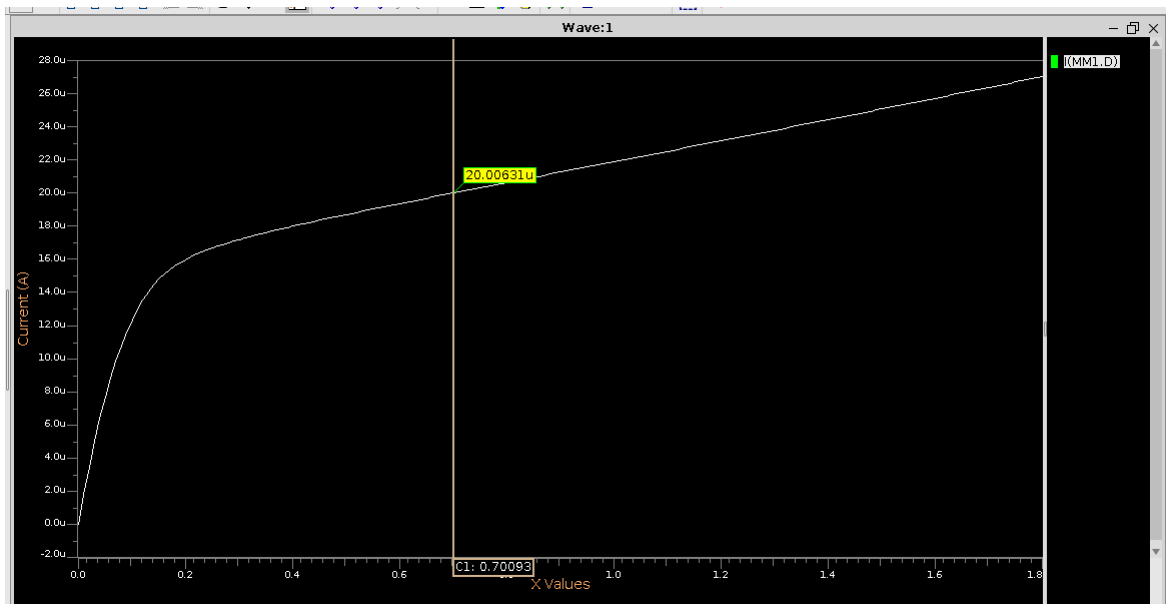


Figure 5: I_d for Basic current mirror circuit

5 Basic current mirror circuit with $3I_{ref}$

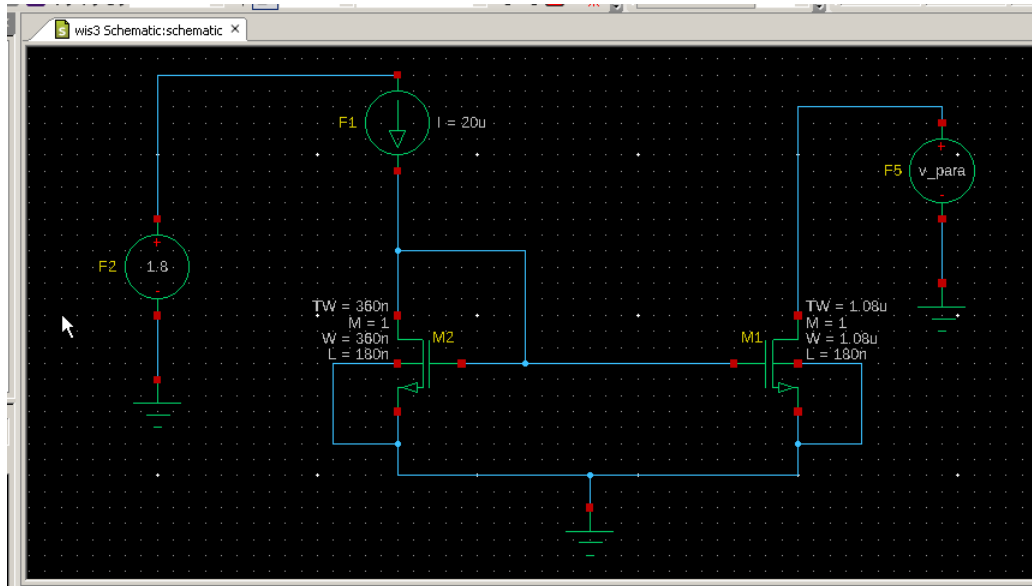


Figure 6: circuit diagram for Basic current mirror circuit with $3I_{ref}$

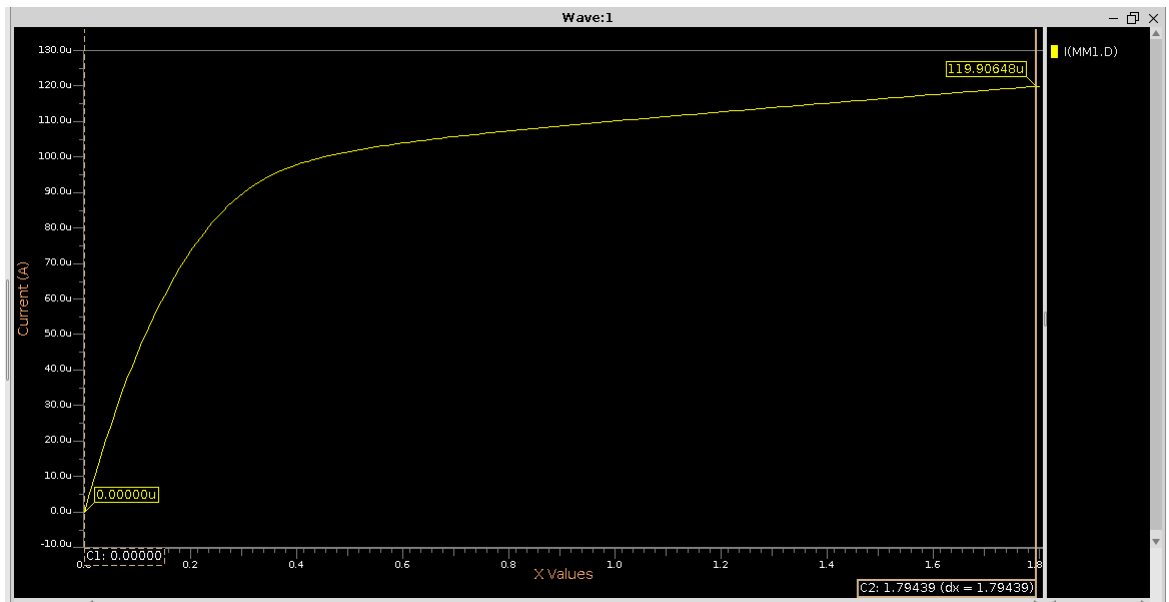


Figure 7: I_d for Basic current mirror circuit with $3I_{ref}$

6 Basic current mirror circuit with $1/3 I_{ref}$

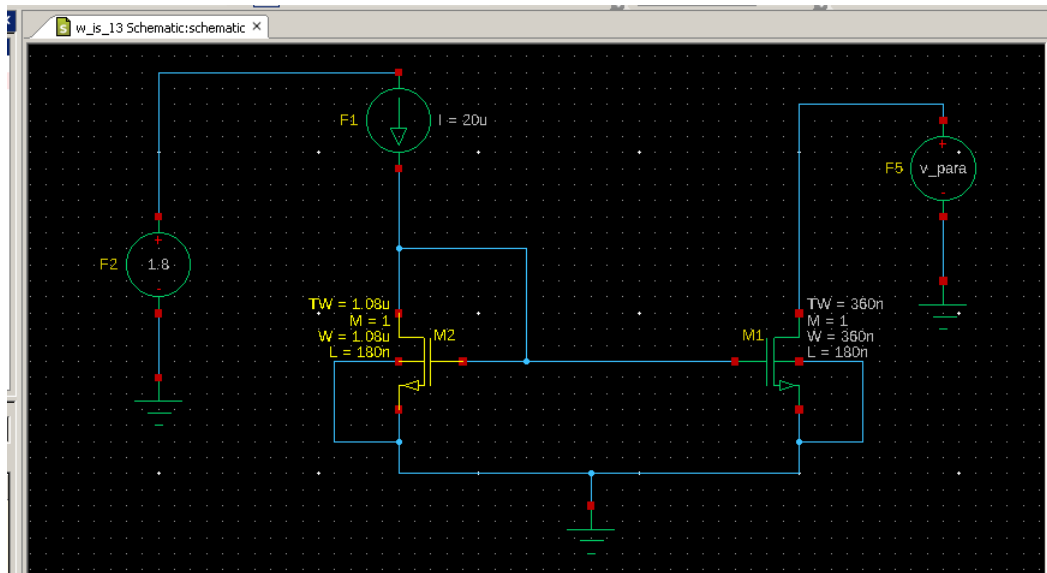


Figure 8: circuit diagram for Basic current mirror circuit with $1/3 I_{ref}$

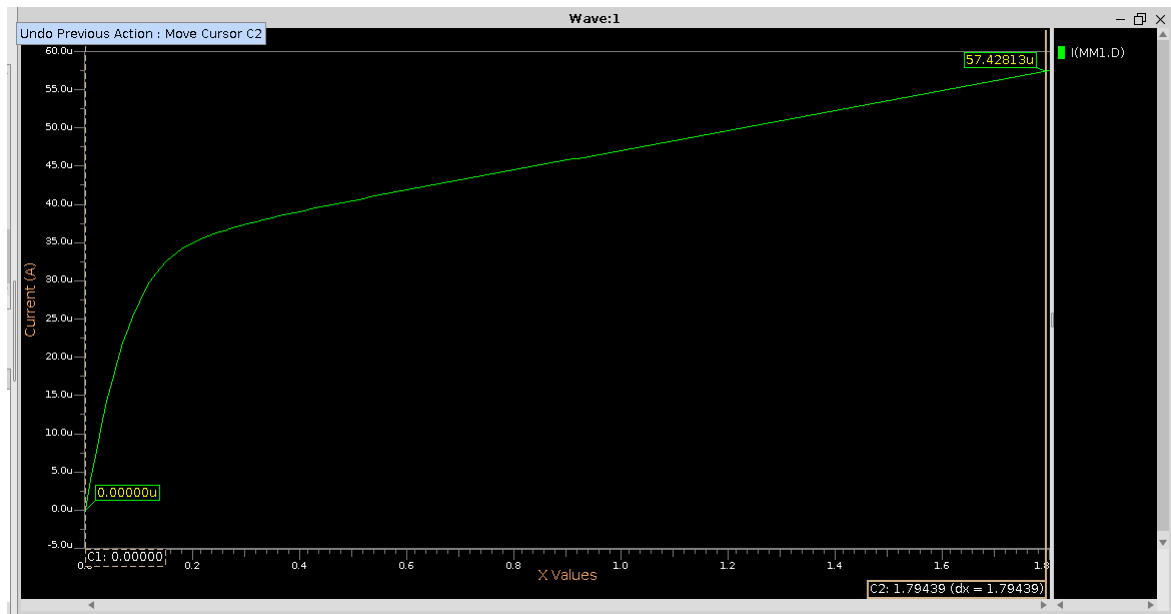


Figure 9: I_d for Basic current mirror circuit with $1/3 I_{ref}$

7 Multiple finger based current mirror circuits

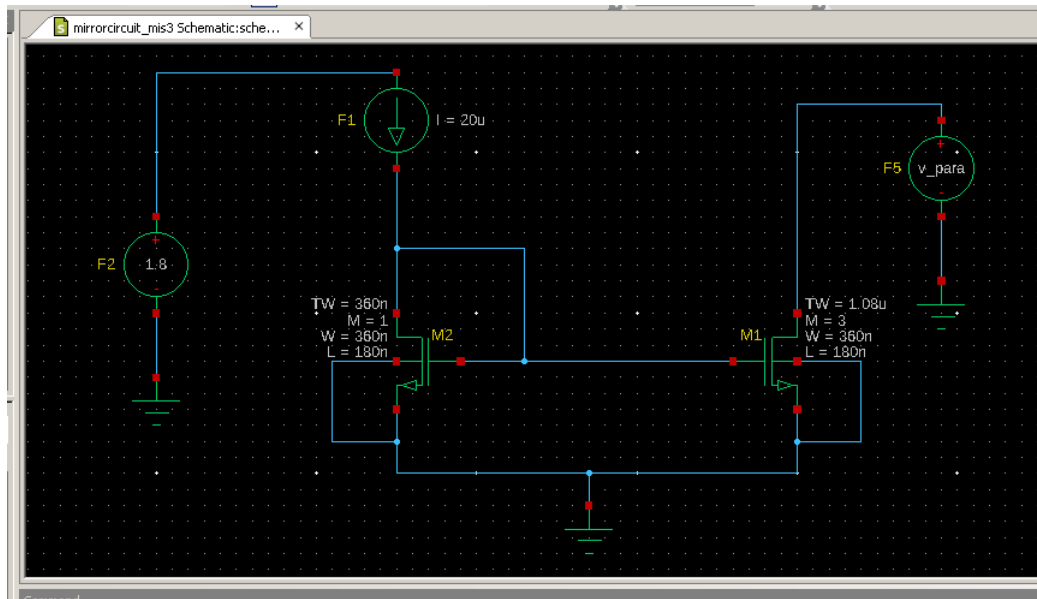


Figure 10: circuit diagram for Basic current mirror circuit with $m=3$ at transistor2

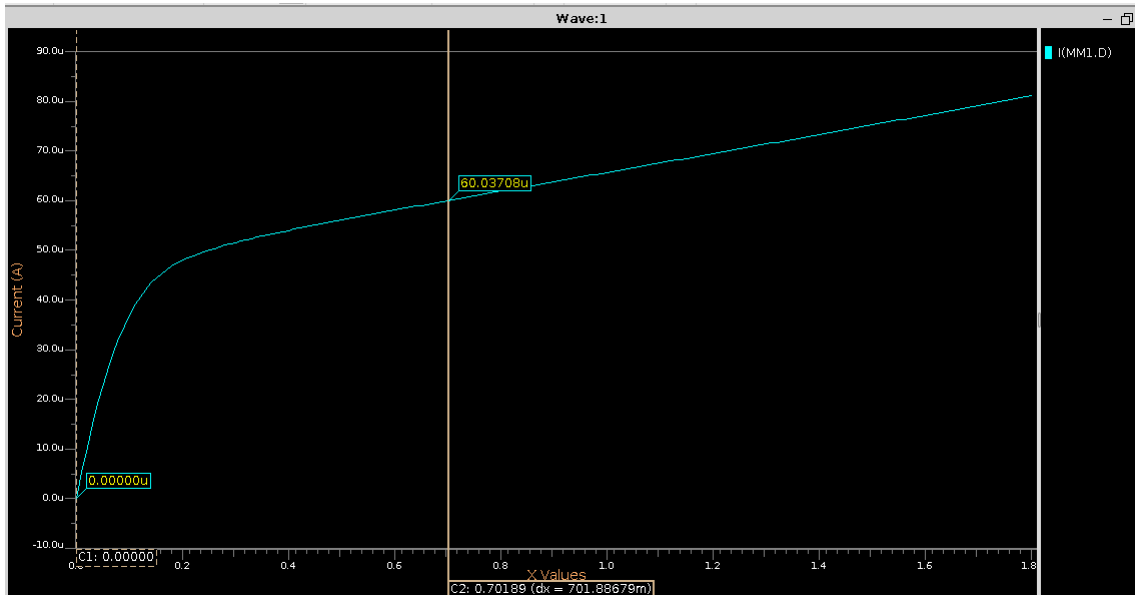


Figure 11: I_d for Basic current mirror circuit with $m=3$ at transistor2

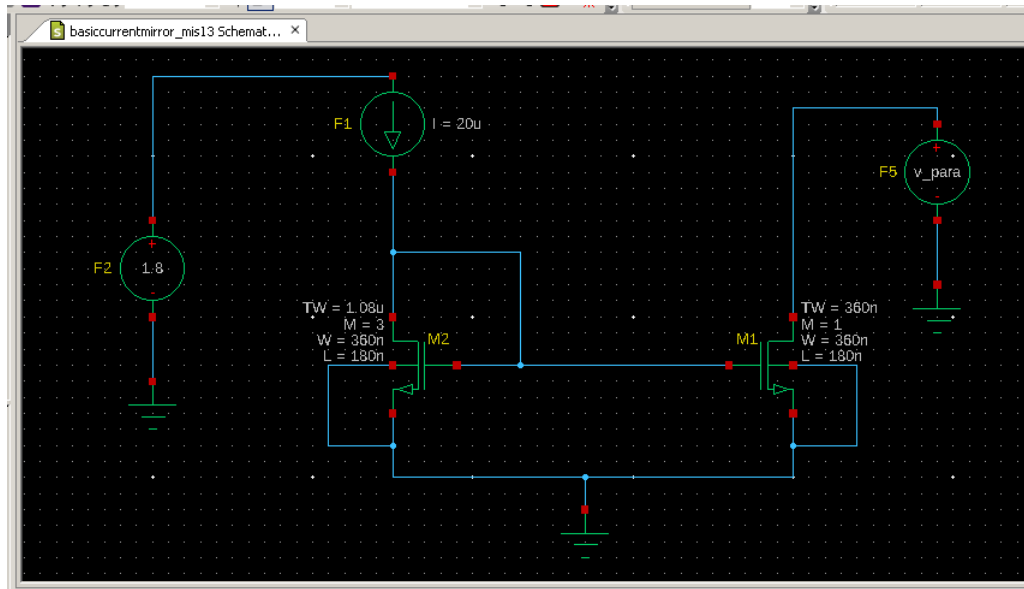


Figure 12: circuit diagram for Basic current mirror circuit with $m=3$ at transistor1

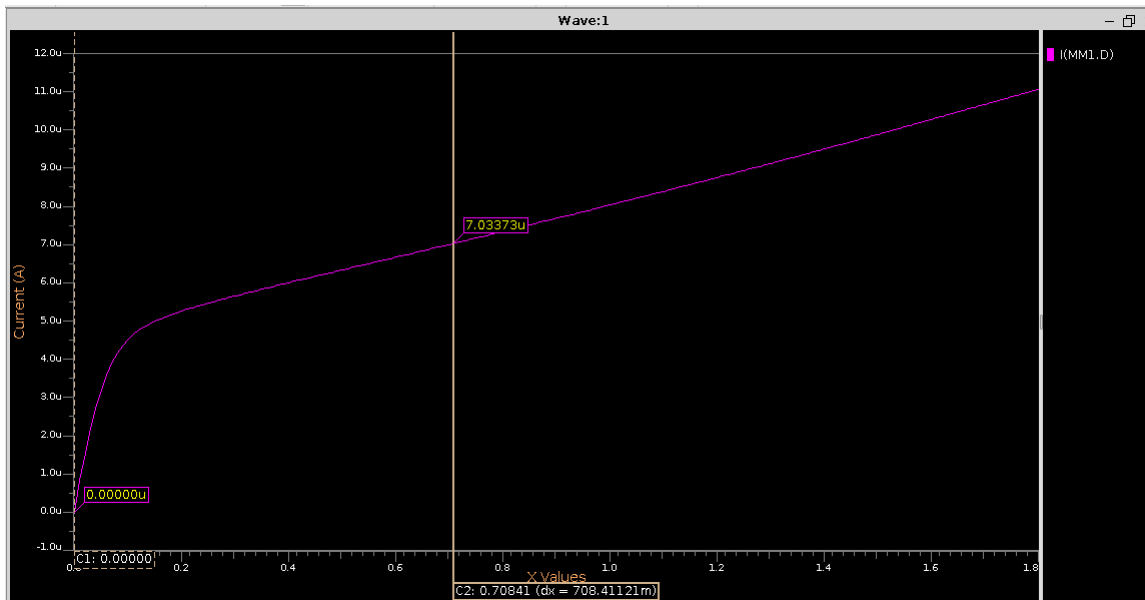


Figure 13: I_d for Basic current mirror circuit with $m=3$ at transistor1

8 Cascoded current mirror circuit

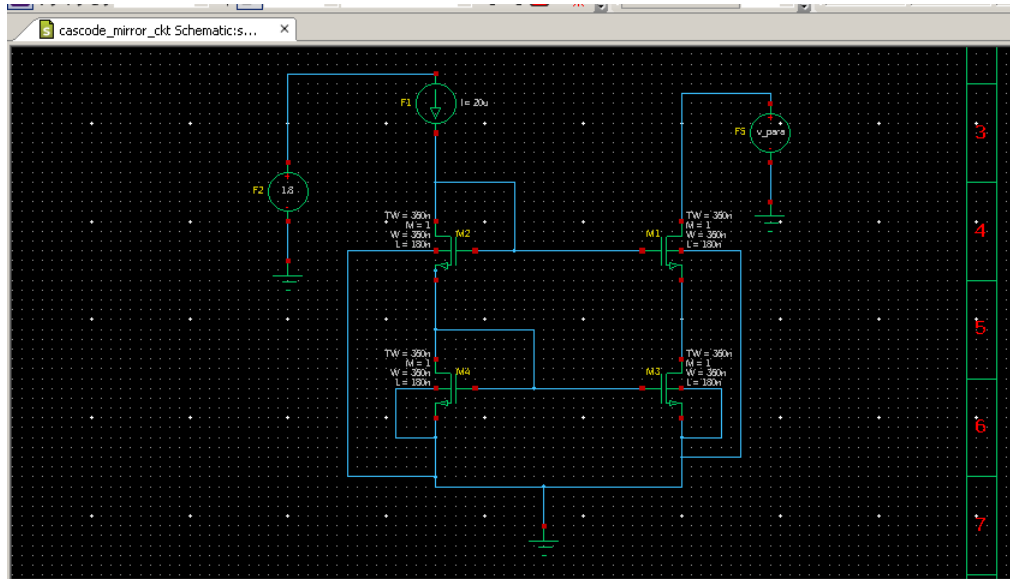


Figure 14: Cascoded current mirror circuit with $m=3$

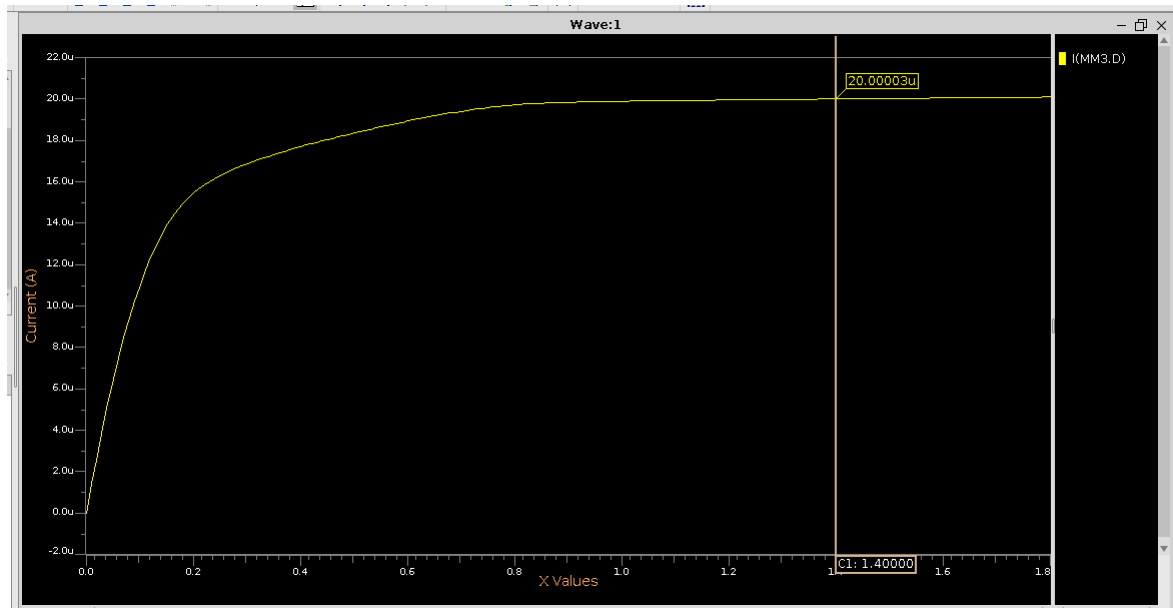


Figure 15: I_d for Cascoded current mirror circuit

9 High swing cascoded current mirror circuit

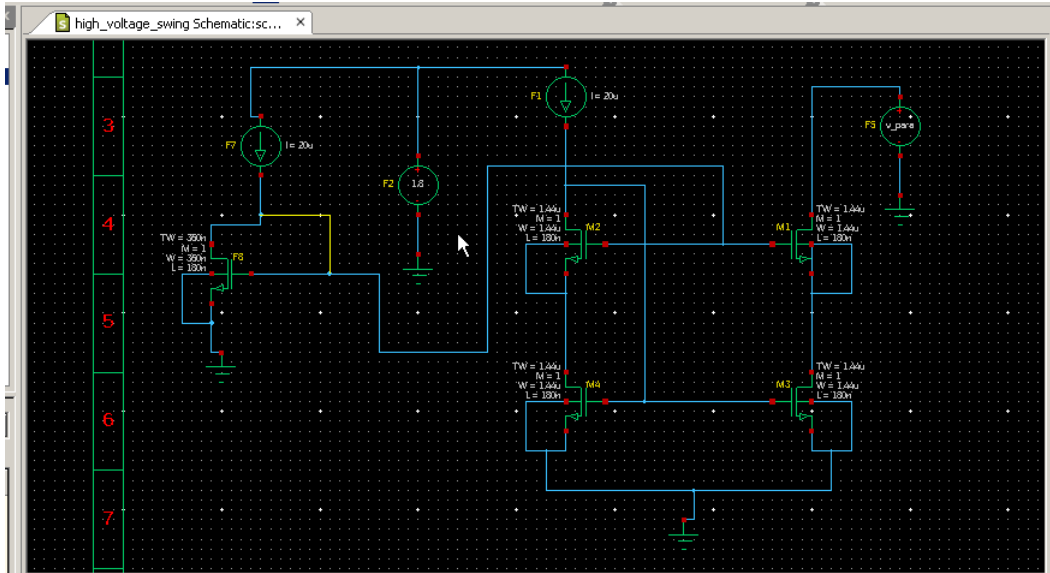


Figure 16: High swing cascoded current mirror circuit with $m=3$

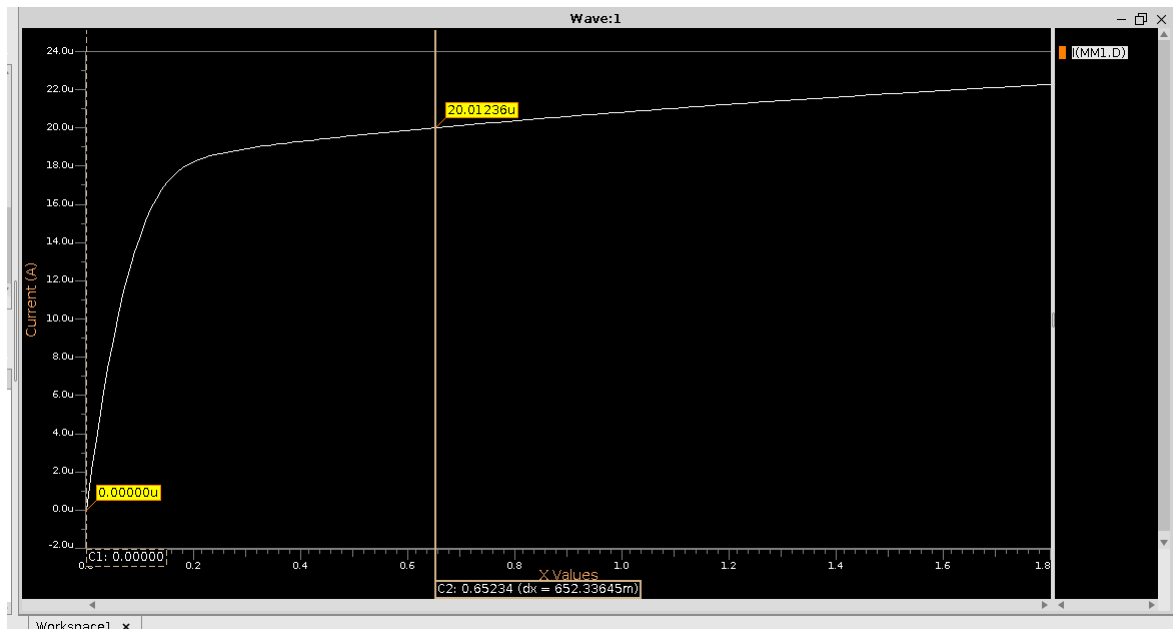


Figure 17: I_d for High swing cascoded current mirror circuit

10 Comparison table

	mirror circuit	I_d u	v of transistor2
	basic mirror ckt	20	0.70093
	basic mirror ckt of (3Iref)	20	0.70093
	basic mirror ckt of (1/3Iref)	20	0.70093
	basic mirror ckt of m is 3	60	0.70189
	basic mirror ckt with mis 1/3	70.377	0.70841
	cascoded mirror ckt	20	1.4000
	High swing cascoded mirror ckt	20	0.65234

11 Conclusions:-

- All the results have been obtained practically and matching with the theoretical justification. The theoretical calculations have been done.
- sic current mirror circuit have good output swing ,but is highly depends on V_{ds}
- By increasing the number of parallel circuits, so we get the same drop on every circuit, therefore if you increase the fingers, we get proper copy current within range.
- The cascode current mirror circuit works properly to eliminate V_{ds} on copy current, however it is reducing the swing.
- if you need stability and best copy of current Cascode circuit is highly preferable,f you need only high swing ,then High swing cascode current mirror circuit ,highly preferable.